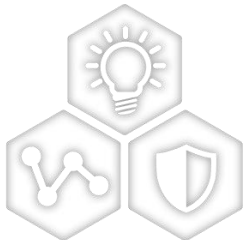


Wireless Guitar Project: Analog



A Leading Provider of Smart, Connected and Secure Embedded Control Solutions




SMART | CONNECTED | SECURE

Sultan Al Niyadi

Project Overview



Project Overview

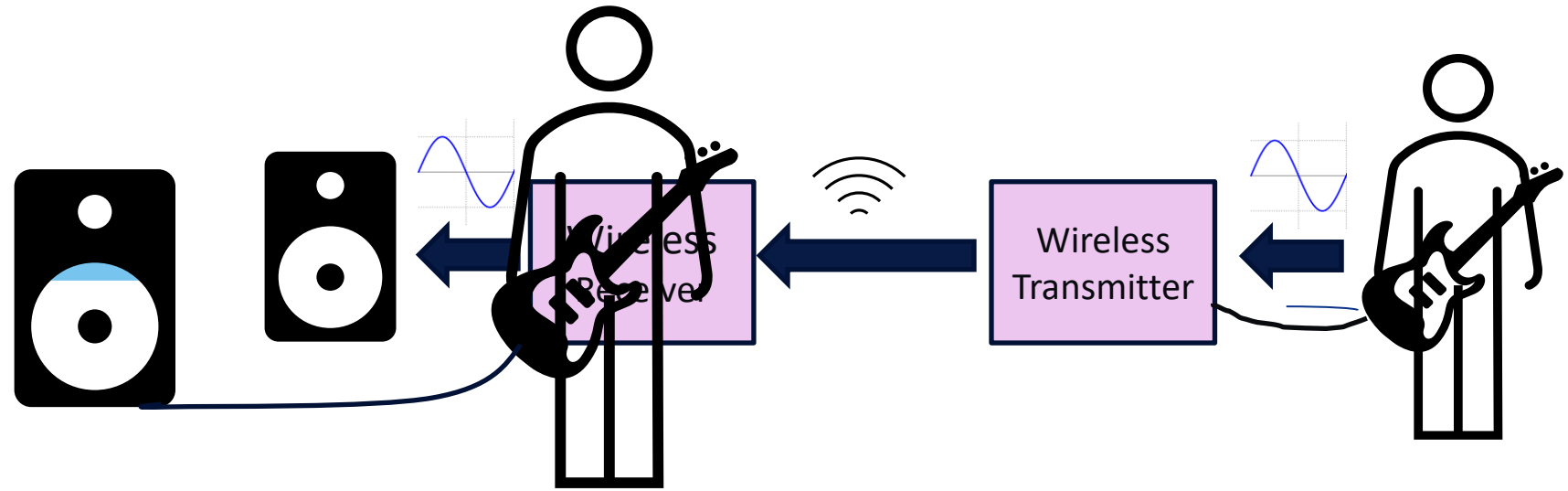


Goal of the Project


- Range up to 20ft-30ft
- Delay < 20ms
- Least possible noise




Transmitter and Receiver

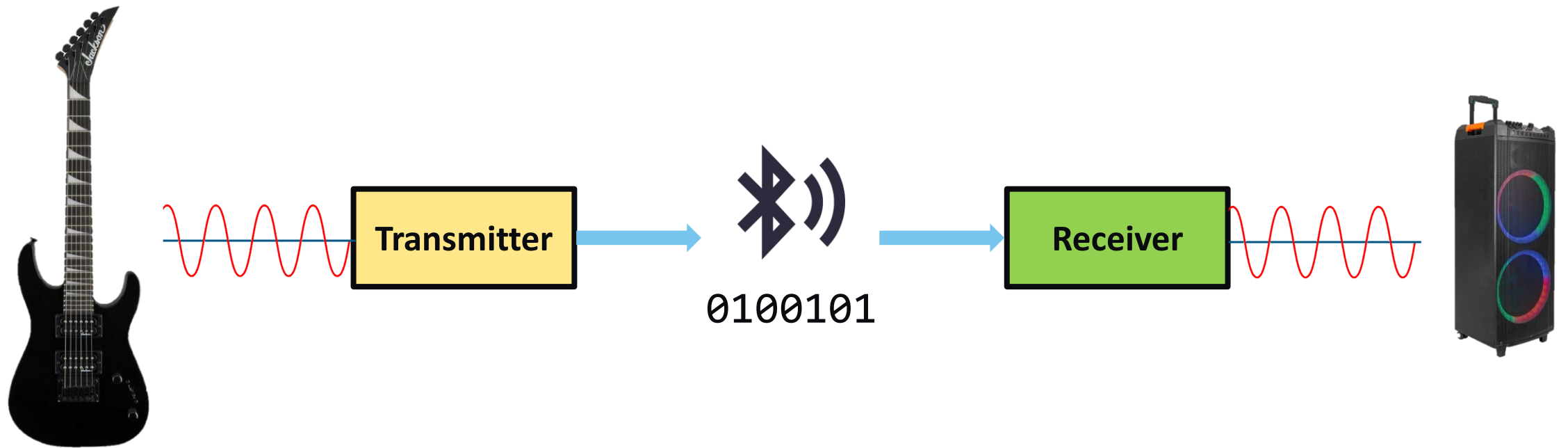

Transmitter

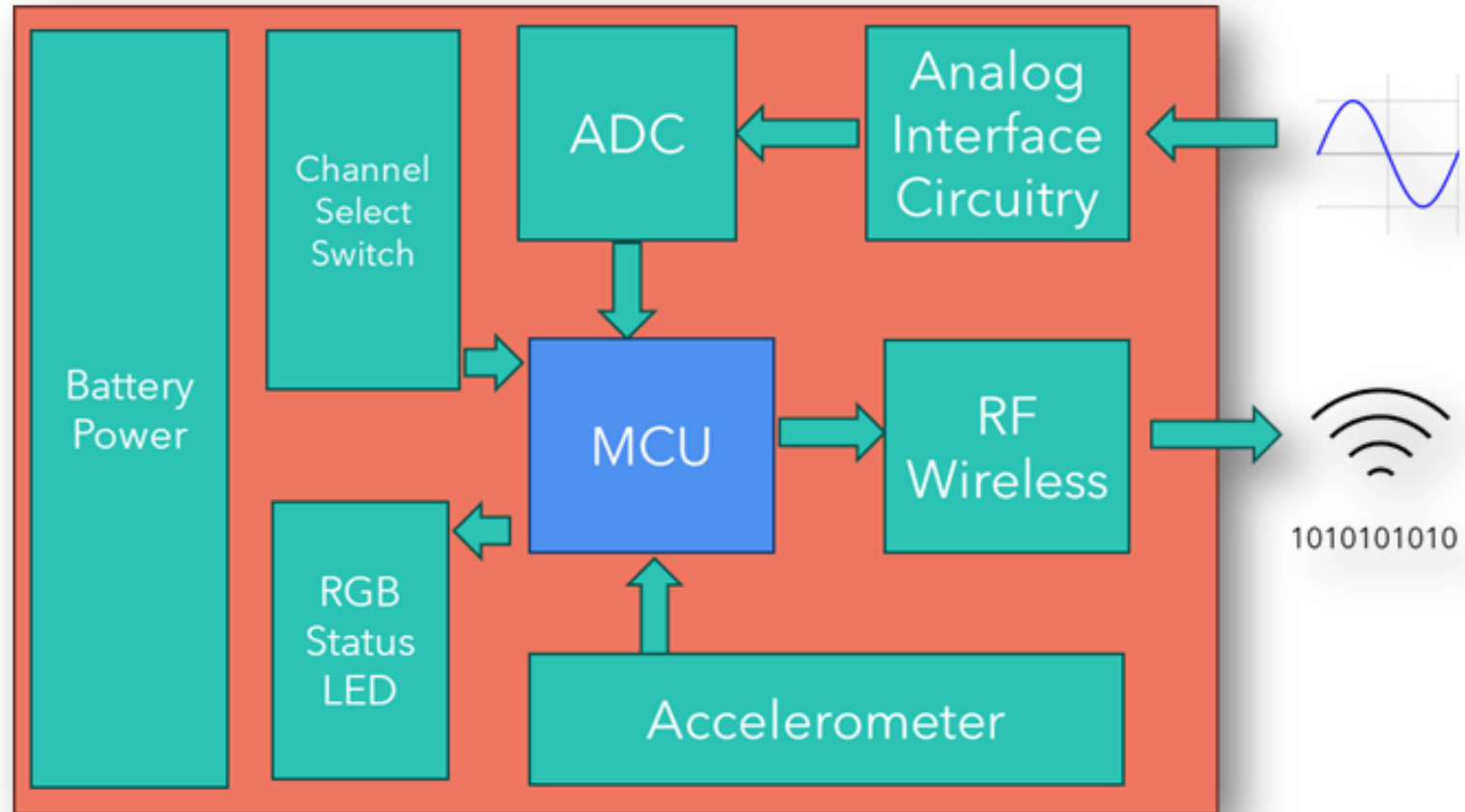


Receiver




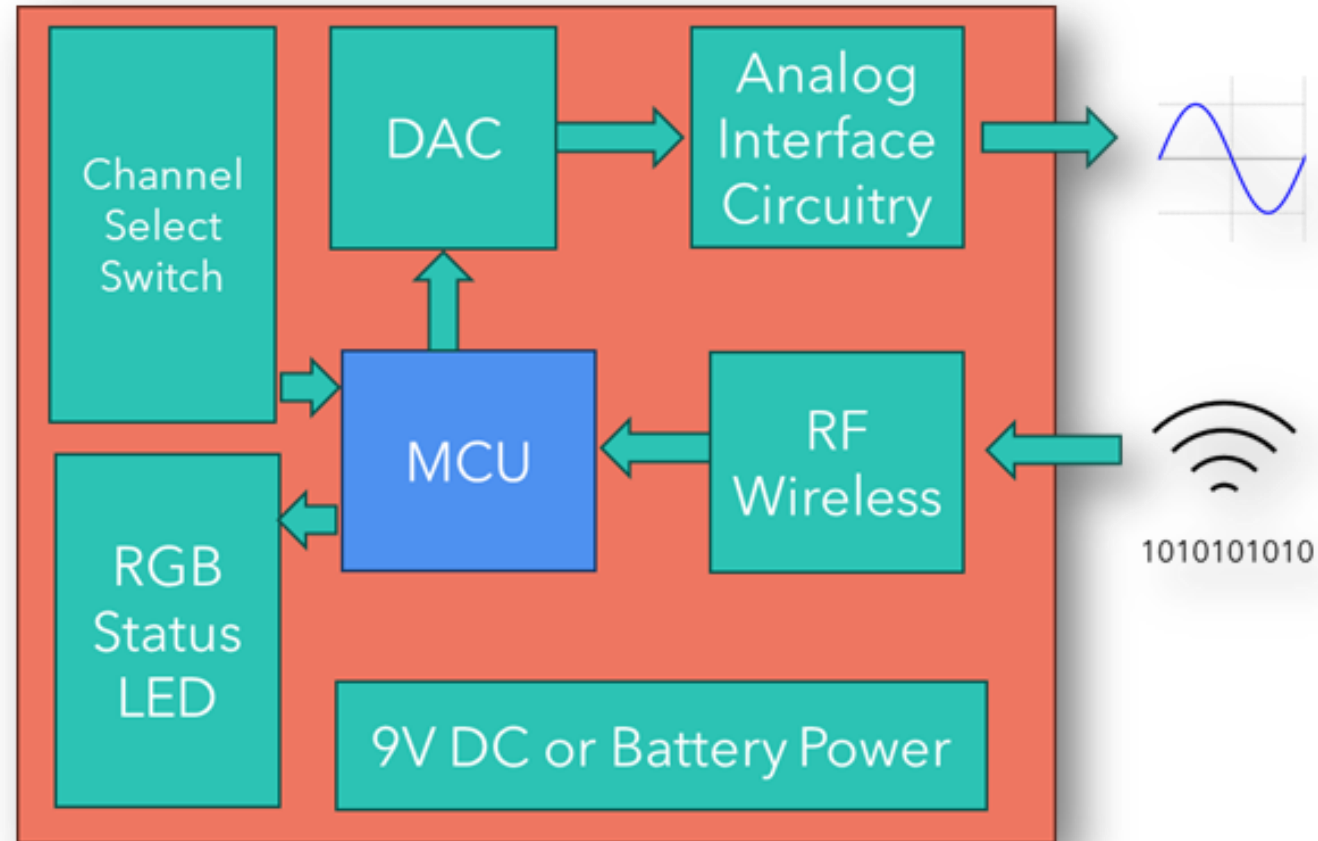


Analog Perspective

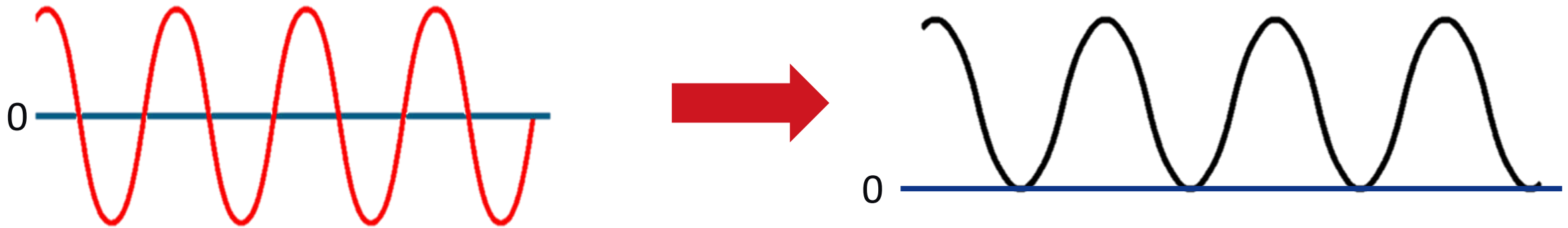Signal Conditioning for ADC (Transmitter)



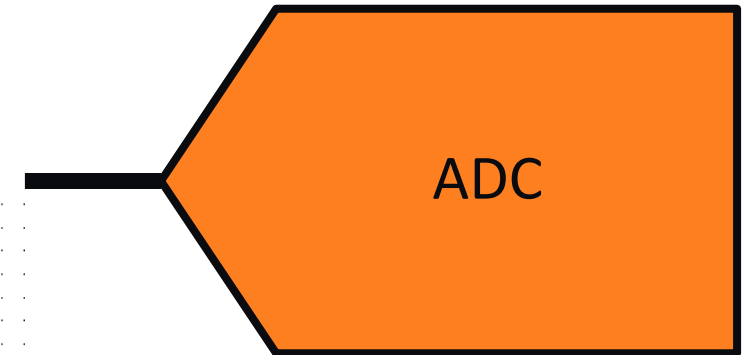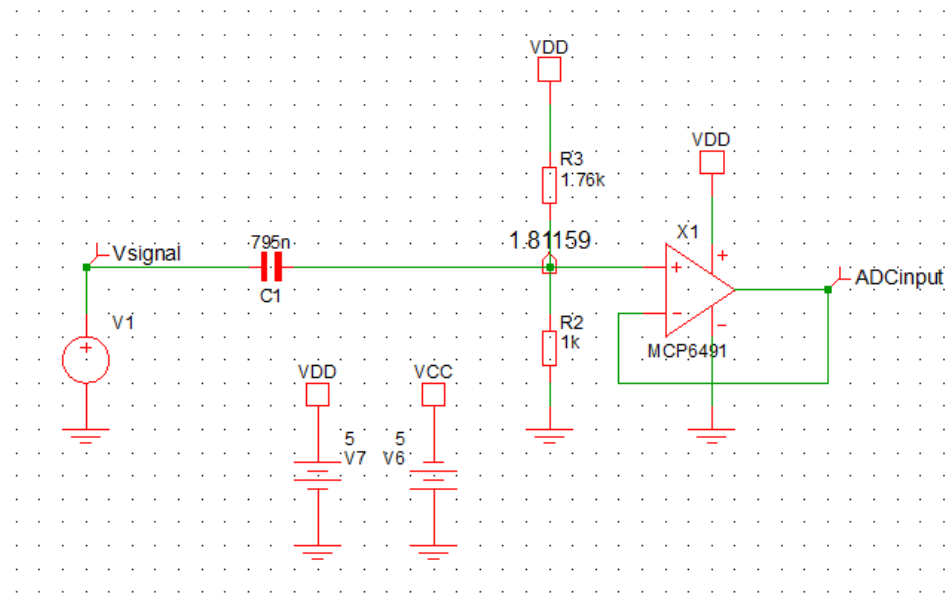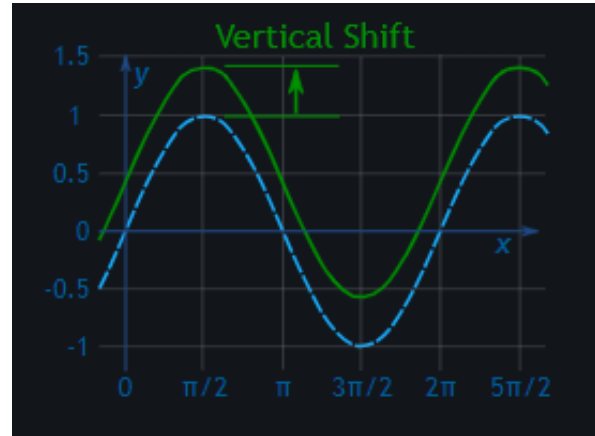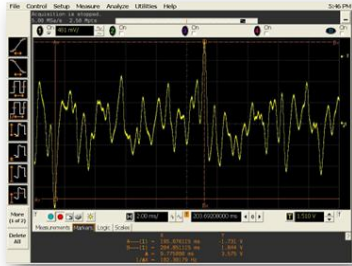
Signal Conditioning for ADC (Transmitter)





ADC

Transmitter Circuit: Mindi

Signal Conditioning for DAC (Receiver)

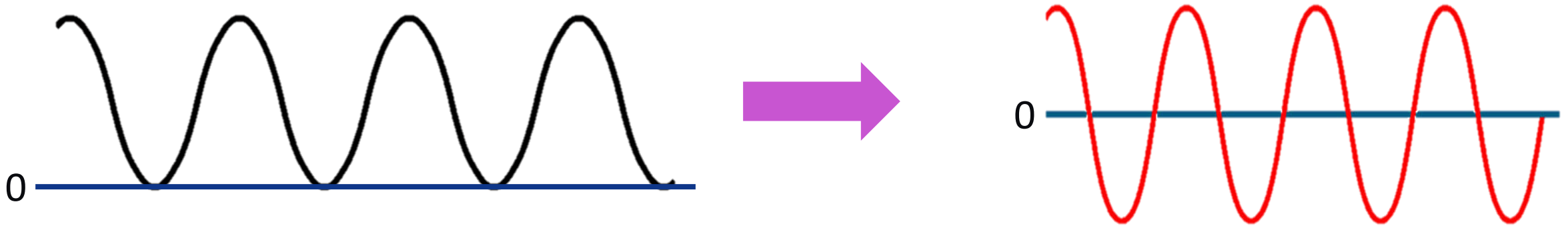

Signal Conditioning for DAC (Receiver)

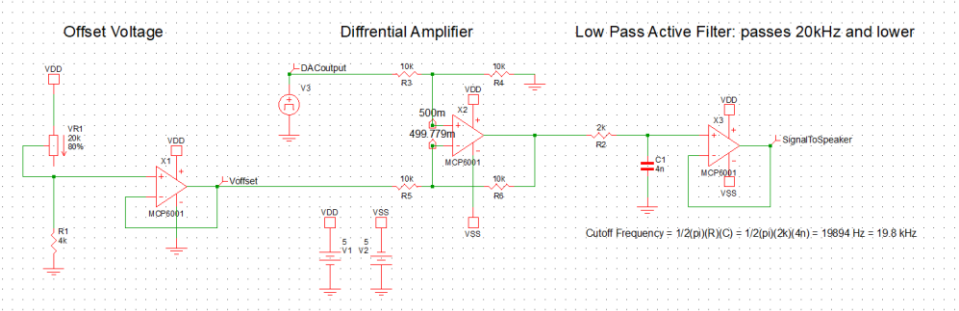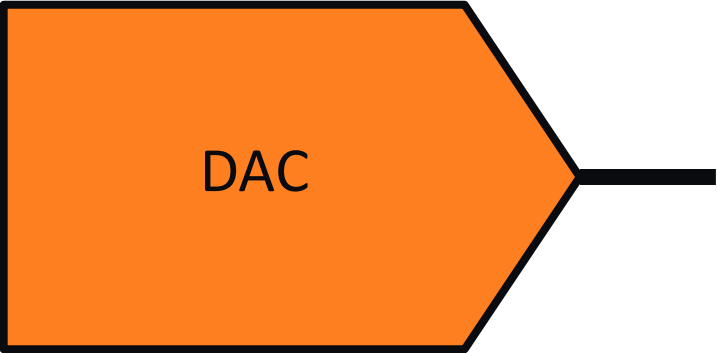

Receiver Circuit: Mindi

Thank you!
